

HDM ASSIGNMENT 1

SUBMITTED BY:

MANOJ KUMAR SINGH

MEC2021027



INDIAN INSTITUTE OF INFORMATION TECHNOLOGY,ALLAHABAD

QUESTION 1: Implement 4 bit ripple carry adder. Optimize the adder for speed. Assume load capacitance to be 50 pF, $V_{DD} = 3.3$ V. You may assume input capacitance to be 2 pF (for the input A [3:0], B [3:0] and C_{in}) if required in the calculation.

 


Fig.1 Basic Full adder with complementary output


 


Fig.2 4 bit ripple carry adder using Fig.1

(A) Detailed calculation and sizing of transistor

For 1-bit adder

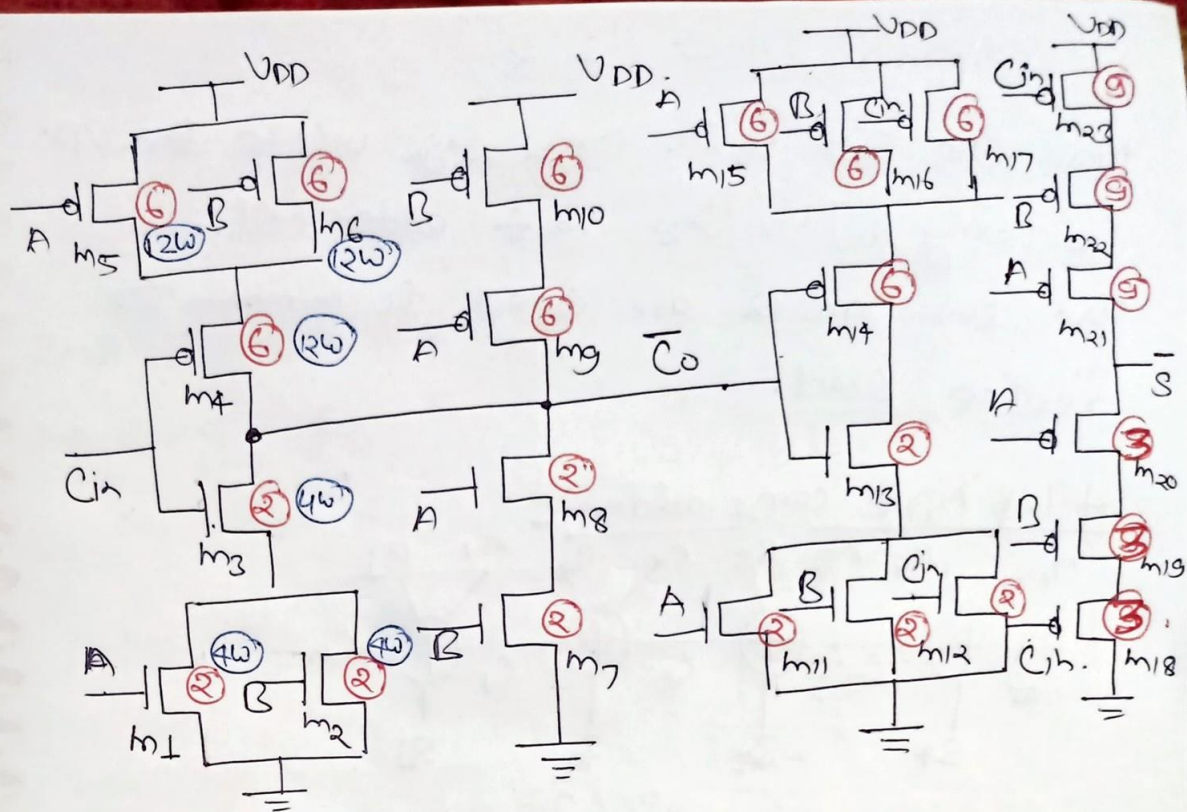

From the MOS model,

$$\eta = \frac{\mu_n}{\mu_p} = \frac{666}{210} = 3.14 \approx 3.$$

$$\therefore (w/L)_p = 4(w/L)_n$$

If the carry ckt. is symmetrically sized, then
 the I/P has a logical effort of 2.
 The optimal stage is 4 (FO4) for minimum
 delay.

$$f = gh \Rightarrow 4 = gh \Rightarrow \therefore h = \frac{4}{2} = 2$$



$$h \text{ (for a stage)} = \frac{\text{Cap of carry stage}}{C_h} = 2$$

\therefore optimal fanout is 2.

Now, the cost of the carry stage will be the I/P.
(or carry in) for the next adder cell.

The sum gates are sized to minimum to reduce load.

4-bit Ripple carry adder :-

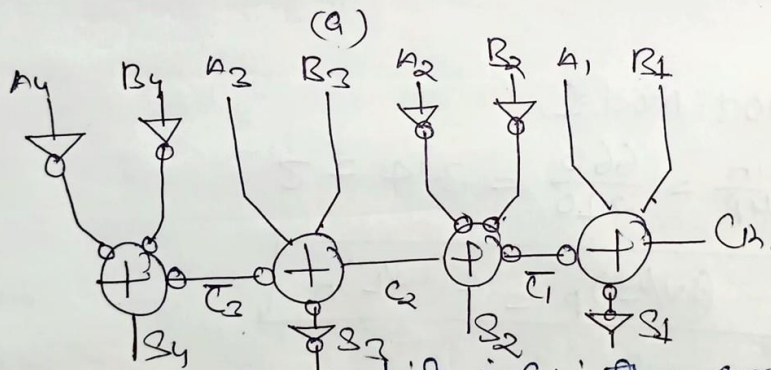 

The carry out of bit i , C_i , is the carry-in to bit $(i+1)$. This carry is said to have twice the weight of the sum S_i . The delay of the adder is set by the time for the carries to ripple through the N -stages, so the $C_0 \rightarrow C_n$ delay should be minimised

$$\therefore M_1 = M_2 = M_3 = 2\left(\frac{W}{L}\right) = 2 \times 2\left(\frac{W}{L}\right) = 4\left(\frac{W}{L}\right) = \frac{4M_n}{4M_n}.$$

$$M_4 = M_5 = M_6 = 2\left(\frac{\omega}{L}\right)_p = 2 \times 6\left(\frac{\omega}{L}\right) = 12\left(\frac{\omega}{L}\right)$$

$$= \frac{12\mu m}{1\mu m}$$

Read all the x-sister. Sizing is same by maintaining the ratio of $M_n:M_p = 3:1$.

$$M_7 = M_8 = 2\left(\frac{\omega}{L}\right)_n = \frac{2\mu m}{1\mu m}$$

$$M_9 = M_{10} = 6\left(\frac{\omega}{L}\right)_p = \frac{6\mu m}{1\mu m}$$

24m Stage :-

$$M_{11} = M_{12} = M_{13} = 2\left(\frac{\omega}{L}\right)_n = \frac{2\mu m}{1\mu m}$$


$$M_{14} = M_{15} = M_{16} = 6\left(\frac{\omega}{L}\right)_p = \frac{6\mu m}{1\mu m}$$

$$M_{18} = M_{19} = M_{20} = 3\left(\frac{\omega}{L}\right)_n = \frac{3\mu m}{1\mu m}$$

$$M_{21} = M_{22} = M_{23} = 9\left(\frac{\omega}{L}\right)_p = \frac{9\mu m}{1\mu m}$$

(B) Schematic and spice netlist

❖ Without optimisation

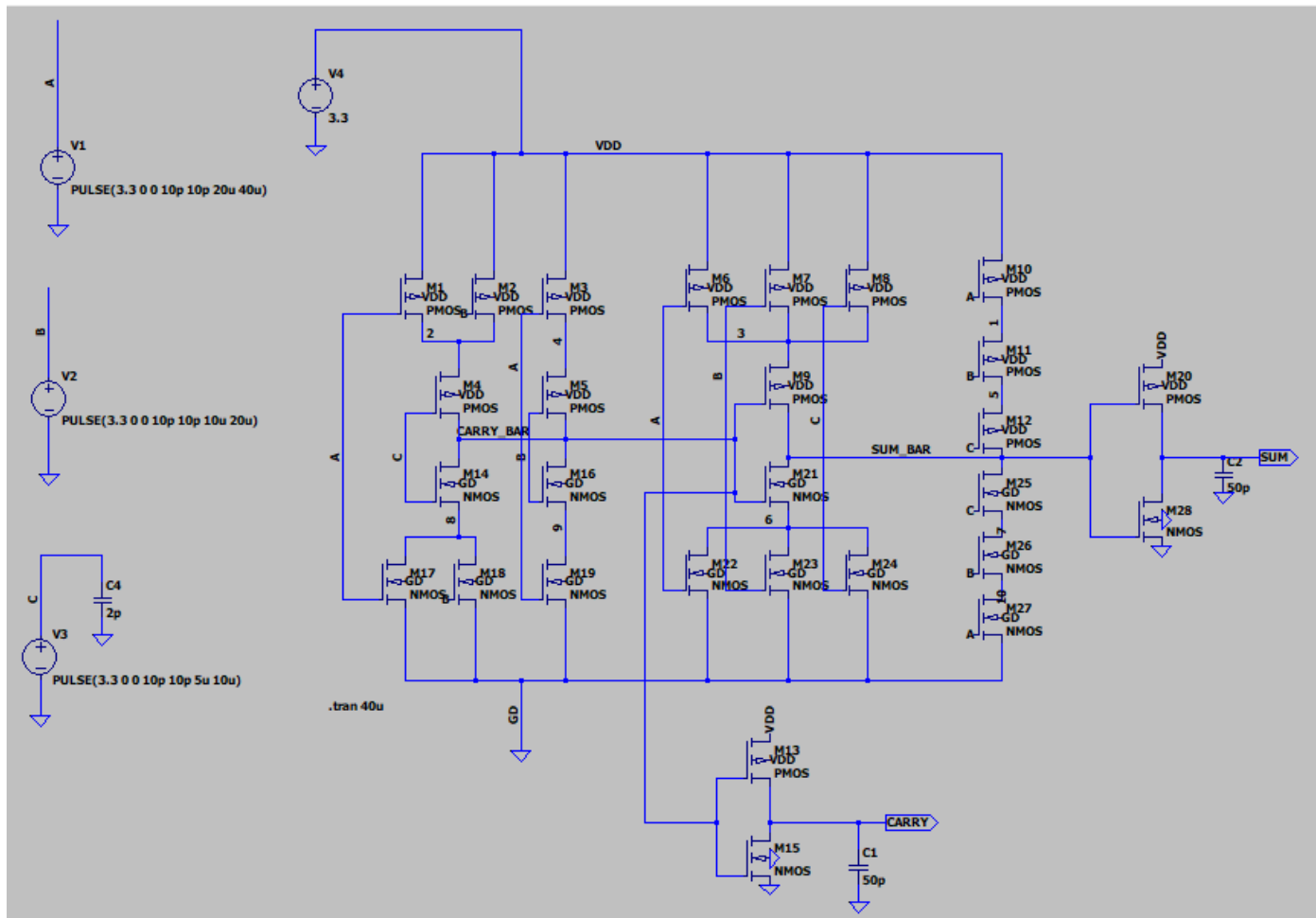

```

M1 VDD A 2 VDD PMOS l=1u w=12u
M2 VDD B 2 VDD PMOS l=1u w=12u
M3 VDD A 4 VDD PMOS l=1u w=6u
M4 2 C CARRY_BAR VDD PMOS l=1u w=12u
M5 4 B CARRY_BAR VDD PMOS l=1u w=6u
M6 VDD A 3 VDD PMOS l=1u w=6u
M7 VDD B 3 VDD PMOS l=1u w=6u
M8 VDD C 3 VDD PMOS l=1u w=6u
M9 3 CARRY_BAR SUM_BAR VDD PMOS l=1u w=6u
M10 VDD A 1 VDD PMOS l=1u w=9u
M11 1 B 5 VDD PMOS l=1u w=9u
M12 5 C SUM_BAR VDD PMOS l=1u w=9u
M14 CARRY_BAR C 8 0 NMOS l=1u w=4u
M16 CARRY_BAR B 9 0 NMOS l=1u w=2u
M17 8 A 0 0 NMOS l=1u w=4u
M18 8 B 0 0 NMOS l=1u w=4u
M19 9 A 0 0 NMOS l=1u w=2u
M21 SUM_BAR CARRY_BAR 6 0 NMOS l=1u w=2u
M22 6 A 0 0 NMOS l=1u w=2u
M23 6 B 0 0 NMOS l=1u w=2u
M24 6 C 0 0 NMOS l=1u w=2u
M25 SUM_BAR C 7 0 NMOS l=1u w=3u
M26 7 B 10 0 NMOS l=1u w=3u
M27 10 A 0 0 NMOS l=1u w=3u

```

```

V1 A 0 PULSE(3.3 0 0 10p 10p 20u 40u)
V2 B 0 PULSE(3.3 0 0 10p 10p 10u 20u)
V3 C 0 PULSE(3.3 0 0 10p 10p 5u 10u)
V4 VDD 0 3.3
C4 C 0 2p


M13 VDD CARRY_BAR CARRY VDD PMOS l=1u w=3u
M15 CARRY CARRY_BAR 0 0 NMOS l=1u w=1u
C1 CARRY 0 50p


M20 VDD SUM_BAR SUM VDD PMOS l=1u w=3u
M28 SUM SUM_BAR 0 0 NMOS l=1u w=1u
C2 SUM 0 50p

.model NMOS NMOS
.model PMOS PMOS
.tran 40u

```

 (c) Simulation results and calculation of delay(unoptimised)




 

Unoptimized carry fall delay=338ns
 Unoptimized carry rise delay=247ns

(B) Schematic and spice netlist

❖ Optimised

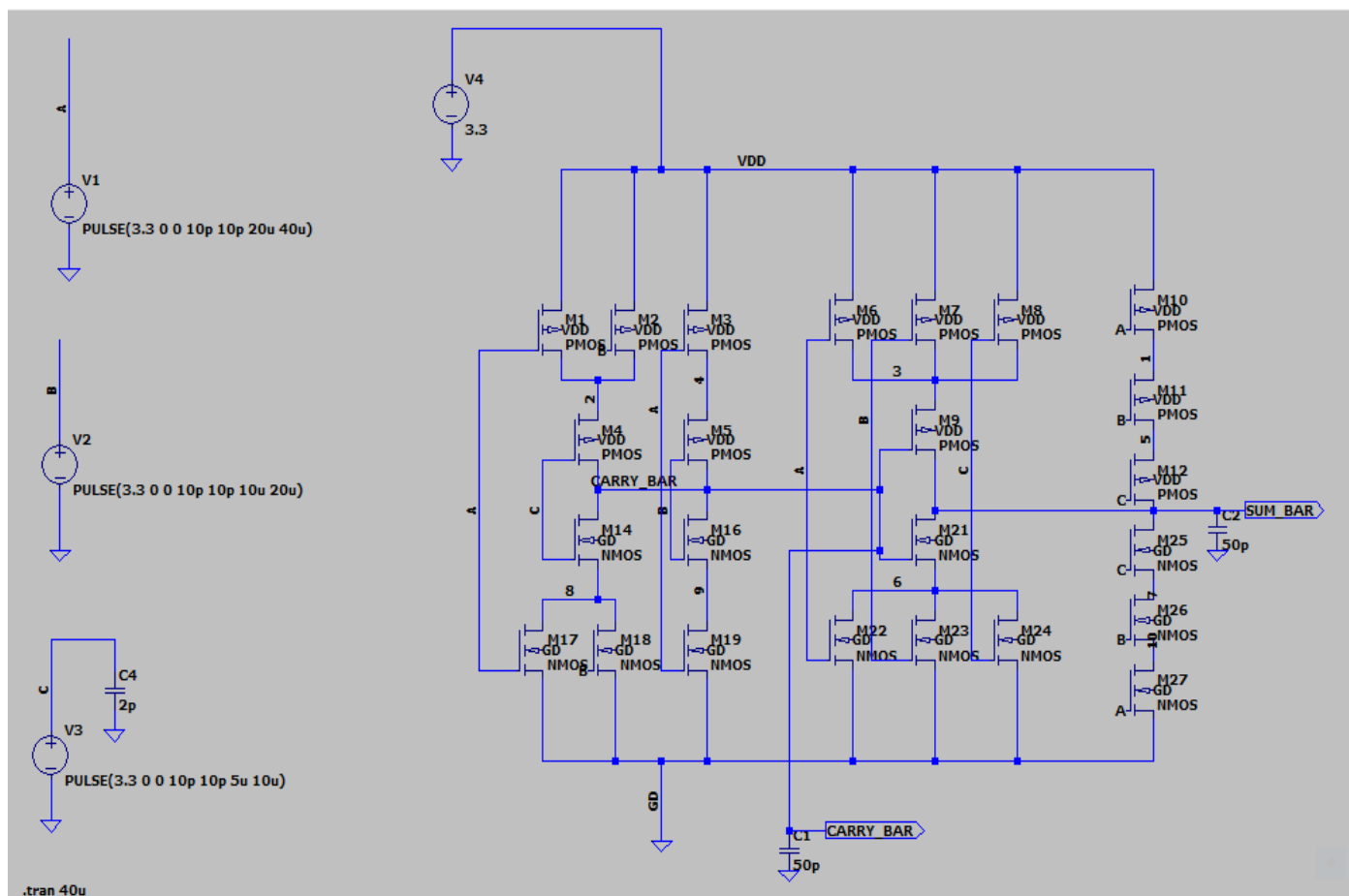


```

M1 VDD A 2 VDD PMOS l=1u w=21u
M2 VDD B 2 VDD PMOS l=1u w=21u
M3 VDD A 4 VDD PMOS l=1u w=6u
M4 2 C CARRY_BAR VDD PMOS l=1u w=21u
M5 4 B CARRY_BAR VDD PMOS l=1u w=6u
M6 VDD A 3 VDD PMOS l=1u w=6u
M7 VDD B 3 VDD PMOS l=1u w=6u
M8 VDD C 3 VDD PMOS l=1u w=6u
M9 3 CARRY_BAR SUM_BAR VDD PMOS l=1u w=6u
M10 VDD A 1 VDD PMOS l=1u w=9u
M11 1 B 5 VDD PMOS l=1u w=9u
M12 5 C SUM_BAR VDD PMOS l=1u w=9u
M14 CARRY_BAR C 8 0 NMOS l=1u w=7u
M16 CARRY_BAR B 9 0 NMOS l=1u w=2u
M17 8 A 0 0 NMOS l=1u w=7u
M18 8 B 0 0 NMOS l=1u w=7u
M19 9 A 0 0 NMOS l=1u w=2u
M21 SUM_BAR CARRY_BAR 6 0 NMOS l=1u w=2u
M22 6 A 0 0 NMOS l=1u w=2u
M23 6 B 0 0 NMOS l=1u w=2u
M24 6 C 0 0 NMOS l=1u w=2u
M25 SUM_BAR C 7 0 NMOS l=1u w=3u
M26 7 B 10 0 NMOS l=1u w=3u
M27 10 A 0 0 NMOS l=1u w=3u

```

```

V1 A 0 PULSE(3.3 0 0 10p 10p 20u 40u)
V2 B 0 PULSE(3.3 0 0 10p 10p 10u 20u)
V3 C 0 PULSE(3.3 0 0 10p 10p 5u 10u)
V4 VDD 0 3.3

```

```

C4 C 0 2p
C1 CARRY_BAR 0 50p
C2 SUM_BAR 0 50p

```

```

.model NMOS NMOS
.model PMOS PMOS


```

```

.tran 40u

```

Delay Calculation :-

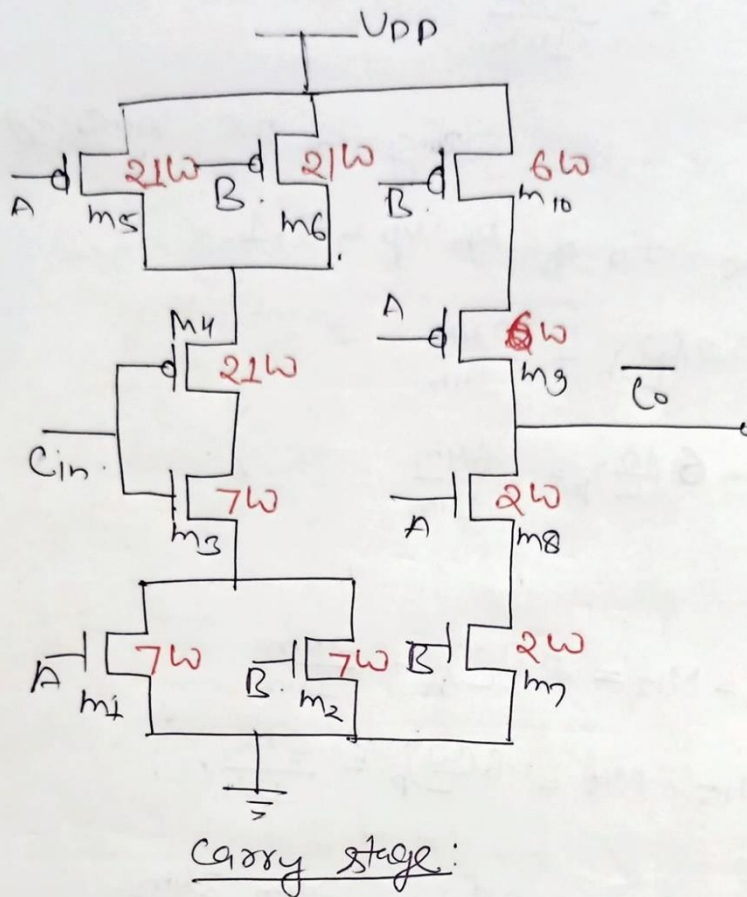

The delay can be reduced by omitting the inverters on the O/Ps. Bcz addition is a self dual function (i.e. the function of complementary I/P is the complementary of the fun.), an inverting, full adder receiving complementary I/P produces true O/Ps. Every other stage operates on complementary data. The delay inverting the adder I/Ps @ sum O/Ps is af the critical ripple carry path.

$$C_L = 50 \text{ pF}$$

$$C_{in} = 2 \text{ pF}$$

$$C_{out} = (6W + 2W) + (6W + 2W) + (9W + 3W).$$

cap. at node $C_{out} = 8W + 8W + 12W$

$$\boxed{C_{out} = 28W}$$

$$\therefore \text{optimal fanout is } 2 \rightarrow \therefore \frac{C_{out}}{C_{in}} = 2$$

$$\therefore \boxed{C_{out} = 2C_{in}}$$



$$\left. \begin{array}{l} C_{out} = 2C_{in} \\ C_{out} = 28W + C_{in} \end{array} \right\} \therefore C_{in} = 28W$$

\therefore The driving transistors (M_1, M_2, \dots, M_6) can thus be sized as:

$$\boxed{M_1 = M_2 = M_3 = 7W = \frac{74\mu\text{m}}{14\mu\text{m}}}$$


$$\boxed{M_4 = M_5 = M_6 = 7W_p = 7(3W) = 21W = \frac{214\mu\text{m}}{14\mu\text{m}}}$$

 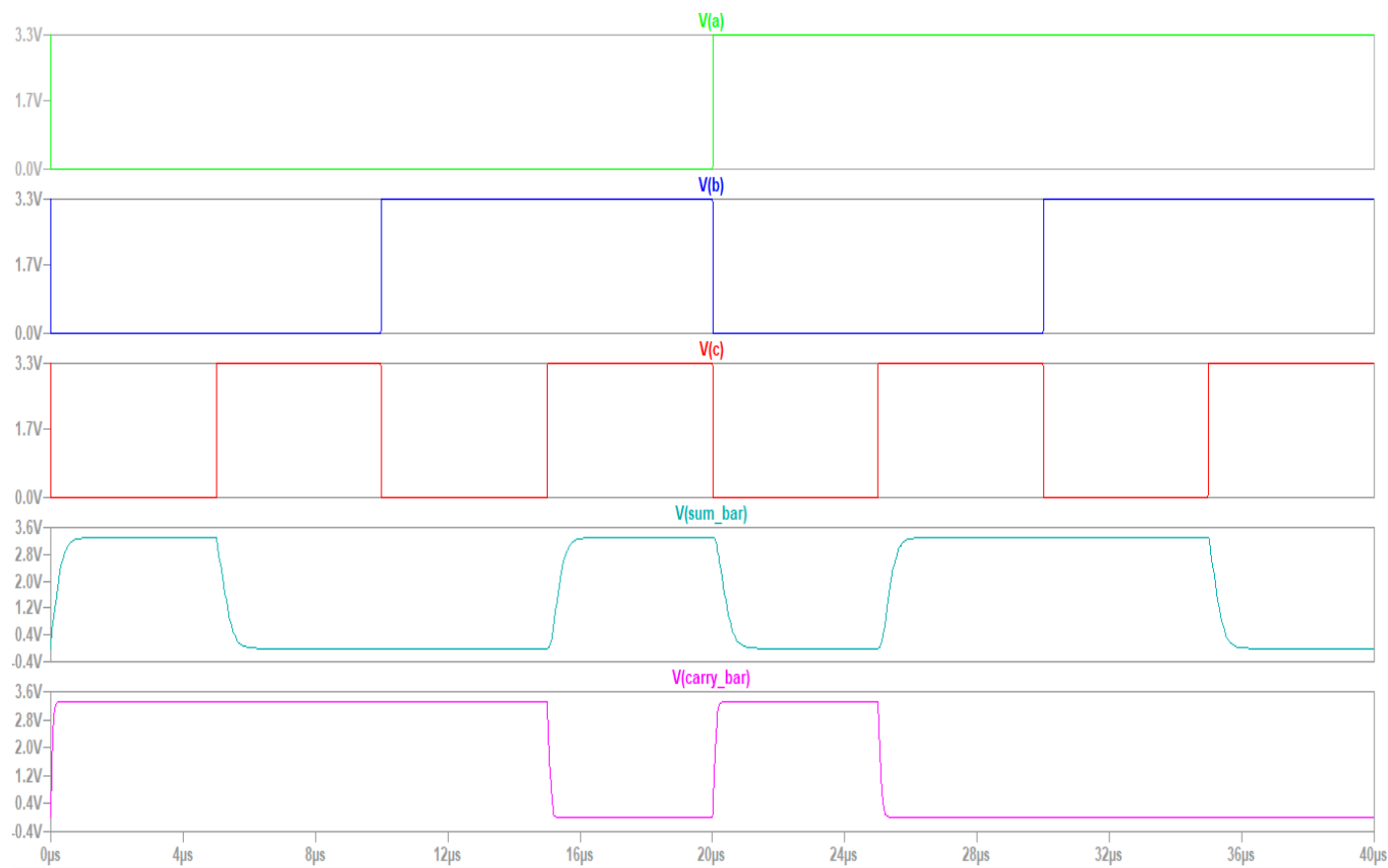(C)Simulation results and calculation of delay(optimised)



Optimised fall delay of carry_bar=71ns

Optimised rise delay of carry_bar=63ns

 

Optimised rise delay of sum_bar=333ns

Optimised fall delay of sum_bar=364ns

BY THE METHOD OF LOGICAL EFFORT

By the method of Logical effort :-

For carry stage,

$$F = GBH.$$

$$= \left(\frac{28W}{4W} \right) \times 1 \times \left(\frac{50pf}{2pf} \right)$$

$$= 7 \times 25$$

$$\boxed{F = 175}$$

For optimum no. of stages,

$$N = \log_4 F$$

$$= \log_4 (175).$$

No. of optimum stages,

$$\boxed{N = 3.72}$$

At $N=4$:

$$\text{delay, } d = NF^{1/N} + P. \quad \text{--- (1)}$$

Parasitic Delay of Inverter.

$$\text{parasitic delay of carry stage} = \frac{(6W+2W) + (6W+2W)}{4W}$$

$$= \frac{16RC}{4RC}$$

$$= 4 P_{inv}.$$

From (1), we have

$$d = 4(175)^{1/4} + 4.$$

$$\boxed{d = 18.542}$$



$$r d N = 43 :-$$

$$d = N(F)^{1/4} + P$$

$$= 3(173)^{1/4} + 3$$

$$|d = 19.78 \text{ z}|$$

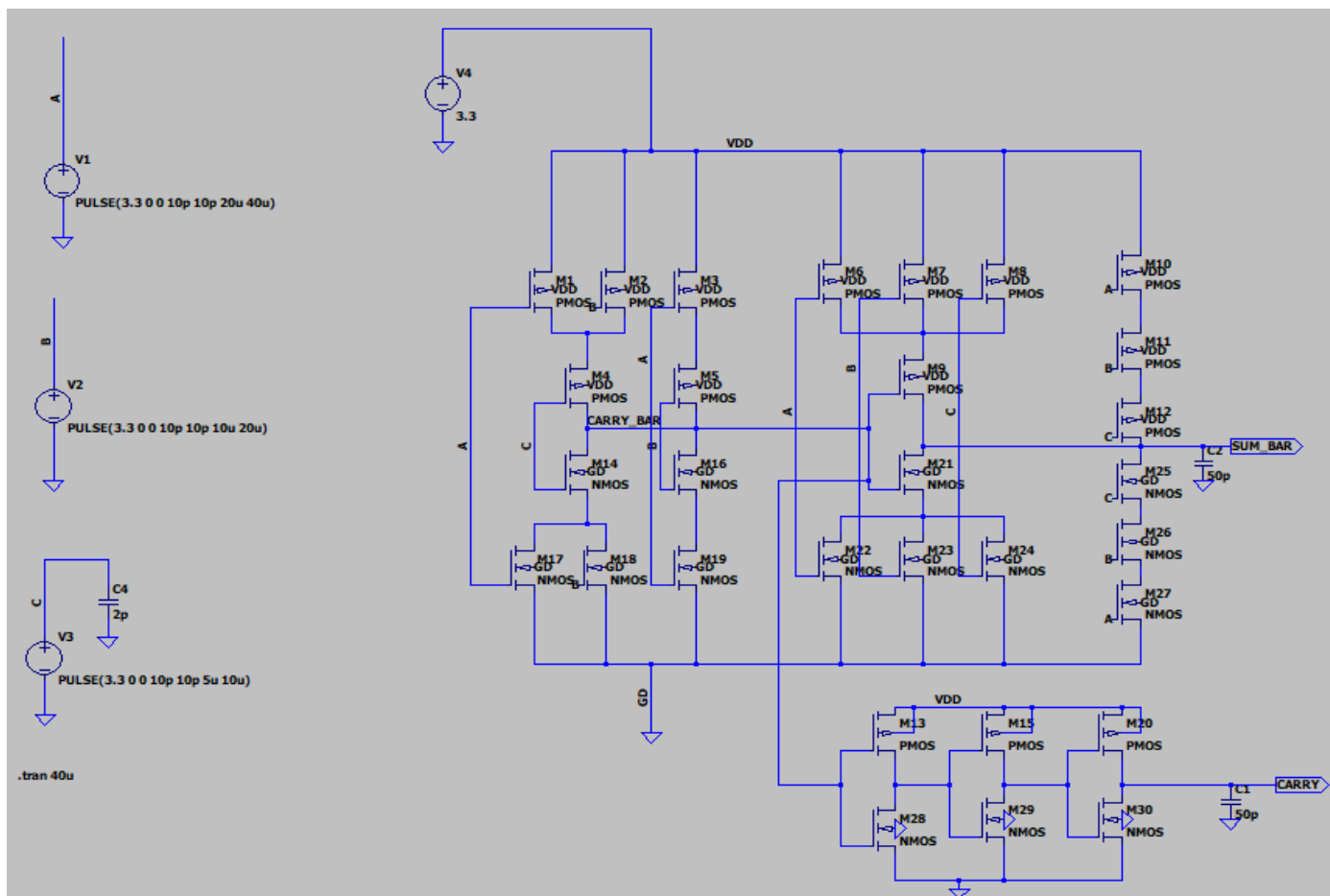 
Delay is least at $N=4$
 \therefore We have to add 3 extra ~~inverter~~ inverter as carry stage already occupied 1 stage.



ADDITION OF INVERTERS

M13 VDD CARRY_BAR N011 VDD PMOS l=1u w=3u
M15 VDD 11 12 VDD PMOS l=1u w=3u
M20 VDD 12 CARRY VDD PMOS l=1u w=3u
M28 11 CARRY_BAR 0 0 NMOS l=1u w=1u
M29 12 11 0 0 NMOS l=1u w=1u
M30 CARRY 12 0 0 NMOS l=1u w=1u


DELAY CALCULATION

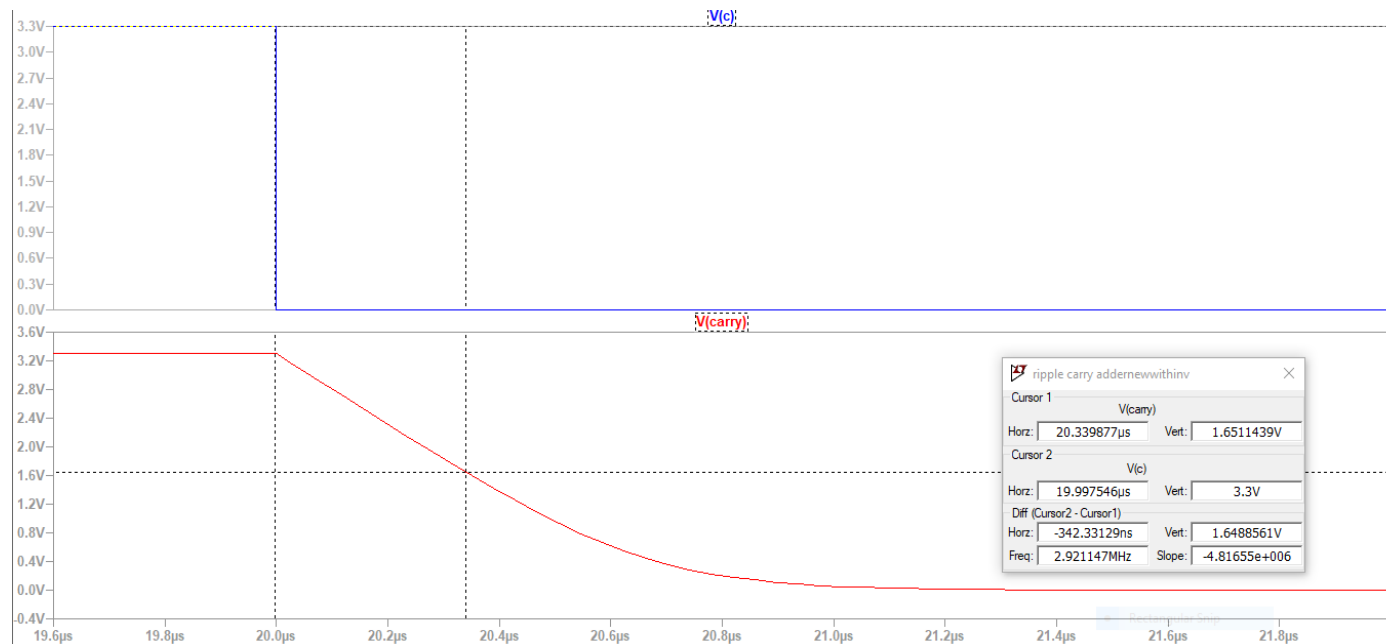



FALL DELAY=342ns

RISE DELAY=247ns

4-bit Ripple Carry Adder

 

(a) Schematic and spice netlist

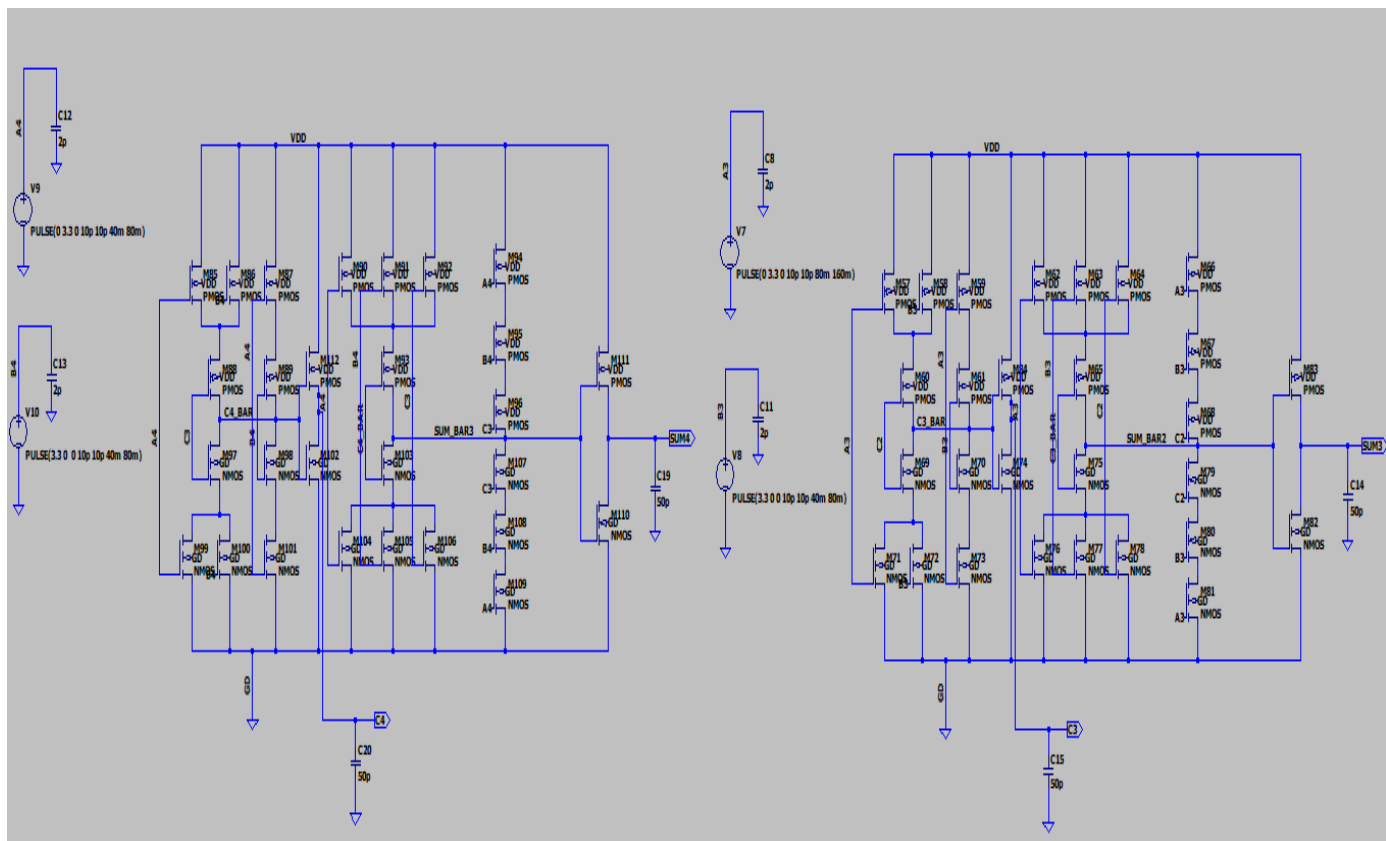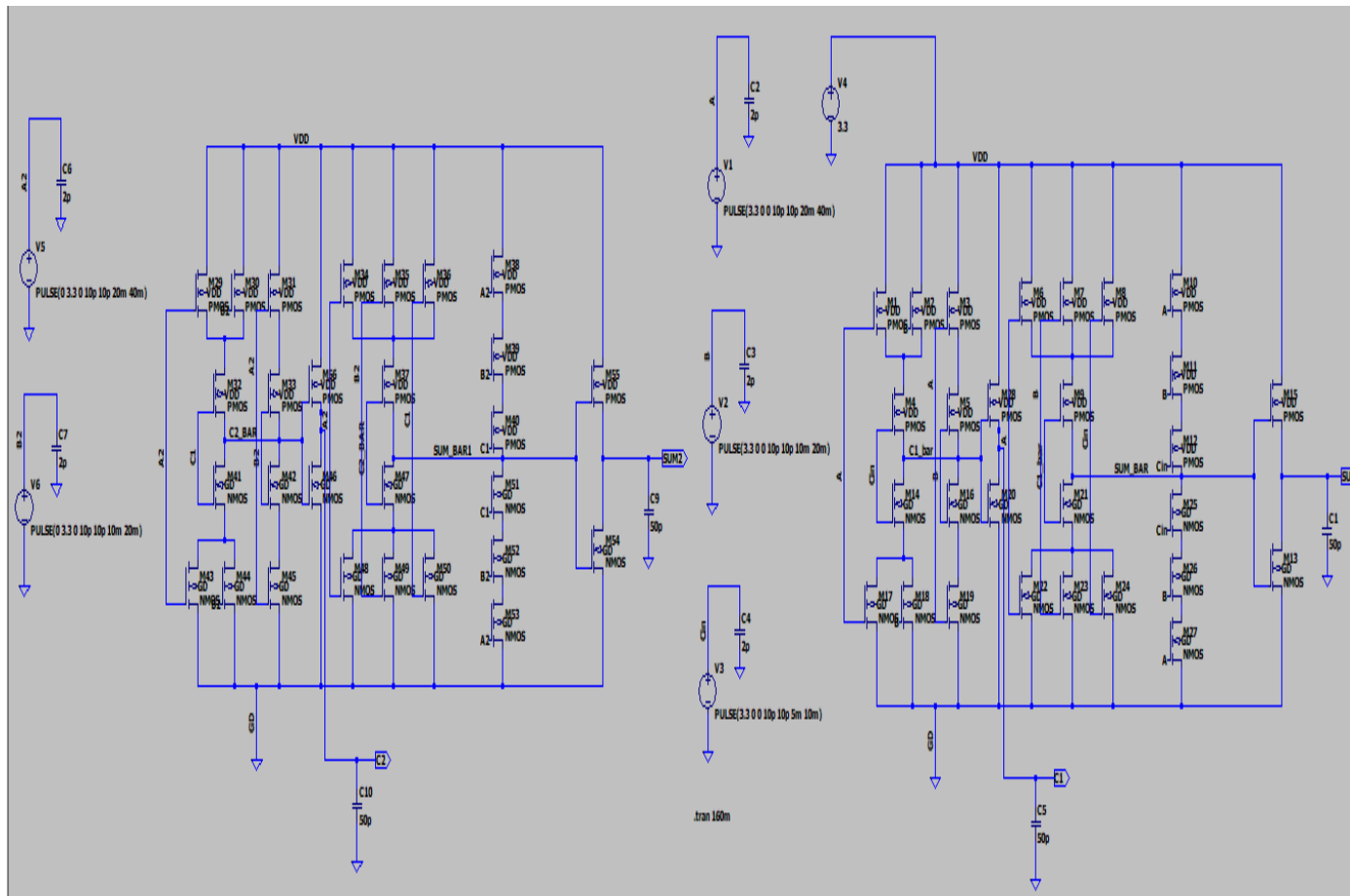

M1 VDD A N013 VDD PMOS l=1u w=6u	V2 B 0 PULSE(3.3 0 0 10p 10p 10m 20m)
M2 VDD B N013 VDD PMOS l=1u w=6u	V3 Cin 0 PULSE(3.3 0 0 10p 10p 5m 10m)
M3 VDD A N017 VDD PMOS l=1u w=6u	V4 VDD 0 3.3
M4 N013 Cin C1_bar VDD PMOS l=1u w=6u	C2 A 0 2p
M5 N017 B C1_bar VDD PMOS l=1u w=6u	C3 B 0 2p
M6 VDD A N014 VDD PMOS l=1u w=6u	C4 Cin 0 2p
M7 VDD B N014 VDD PMOS l=1u w=6u	C1 SUM 0 50p
M8 VDD Cin N014 VDD PMOS l=1u w=6u	C5 C1 0 50p
M9 N014 C1_bar SUM_BAR VDD PMOS l=1u w=6u	M29 VDD A2 N008 VDD PMOS l=1u w=6u
M10 VDD A N011 VDD PMOS l=1u w=9u	M30 VDD B2 N008 VDD PMOS l=1u w=6u
M11 N011 B N020 VDD PMOS l=1u w=9u	M31 VDD A2 N015 VDD PMOS l=1u w=6u
M12 N020 Cin SUM_BAR VDD PMOS l=1u w=9u	M32 N008 C1 C2_BAR VDD PMOS l=1u w=6u
M14 C1_bar Cin N035 0 NMOS l=1u w=2u	M33 N015 B2 C2_BAR VDD PMOS l=1u w=6u
M16 C1_bar B N037 0 NMOS l=1u w=2u	M34 VDD A2 N009 VDD PMOS l=1u w=6u
M17 N035 A 0 0 NMOS l=1u w=2u	M35 VDD B2 N009 VDD PMOS l=1u w=6u
M18 N035 B 0 0 NMOS l=1u w=2u	M36 VDD C1 N009 VDD PMOS l=1u w=6u
M19 N037 A 0 0 NMOS l=1u w=2u	M37 N009 C2_BAR SUM_BAR1 VDD PMOS l=1u w=6u
M20 C1 C1_bar 0 0 NMOS l=1u w=1u	M38 VDD A2 N007 VDD PMOS l=1u w=9u
M21 SUM_BAR C1_bar N032 0 NMOS l=1u w=2u	M39 N007 B2 N019 VDD PMOS l=1u w=9u
M22 N032 A 0 0 NMOS l=1u w=2u	M40 N019 C1 SUM_BAR1 VDD PMOS l=1u w=9u
M23 N032 B 0 0 NMOS l=1u w=2u	M41 C2_BAR C1 N030 0 NMOS l=1u w=2u
M24 N032 Cin 0 0 NMOS l=1u w=2u	M42 C2_BAR B2 N034 0 NMOS l=1u w=2u
M25 SUM_BAR Cin N033 0 NMOS l=1u w=3u	M43 N030 A2 0 0 NMOS l=1u w=2u
M26 N033 B N040 0 NMOS l=1u w=3u	M44 N030 B2 0 0 NMOS l=1u w=2u
M27 N040 A 0 0 NMOS l=1u w=3u	M45 N034 A2 0 0 NMOS l=1u w=2u
M13 SUM SUM_BAR 0 0 NMOS l=1u w=1u	M46 C2 C2_BAR 0 0 NMOS l=1u w=1u
M15 VDD SUM_BAR SUM VDD PMOS l=1u w=3u	M47 SUM_BAR1 C2_BAR N027 0 NMOS l=1u w=2u
M28 VDD C1_bar C1 VDD PMOS l=1u w=3u	M48 N027 A2 0 0 NMOS l=1u w=2u
V1 A 0 PULSE(3.3 0 0 10p 10p 20m 40m)	M49 N027 B2 0 0 NMOS l=1u w=2u
	M50 N027 C1 0 0 NMOS l=1u w=2u

M51 SUM_BAR1 C1 N028 0 NMOS l=1u w=3u
M52 N028 B2 N039 0 NMOS l=1u w=3u
M53 N039 A2 0 0 NMOS l=1u w=3u
M54 SUM2 SUM_BAR1 0 0 NMOS l=1u w=1u
M55 VDD SUM_BAR1 SUM2 VDD PMOS l=1u w=3u
M56 VDD C2_BAR C2 VDD PMOS l=1u w=3u
C9 SUM2 0 50p
C10 C2 0 50p
M57 VDD A3 N005 VDD PMOS l=1u w=6u
M58 VDD B3 N005 VDD PMOS l=1u w=6u
M59 VDD A3 N012 VDD PMOS l=1u w=6u
M60 N005 C2 C3_BAR VDD PMOS l=1u w=6u
M61 N012 B3 C3_BAR VDD PMOS l=1u w=6u
M62 VDD A3 N006 VDD PMOS l=1u w=6u
M63 VDD B3 N006 VDD PMOS l=1u w=6u
M64 VDD C2 N006 VDD PMOS l=1u w=6u
M65 N006 C3_BAR SUM_BAR2 VDD PMOS l=1u w=6u
M66 VDD A3 N004 VDD PMOS l=1u w=9u
M67 N004 B3 N018 VDD PMOS l=1u w=9u
M68 N018 C2 SUM_BAR2 VDD PMOS l=1u w=9u
M69 C3_BAR C2 N026 0 NMOS l=1u w=2u
M70 C3_BAR B3 N031 0 NMOS l=1u w=2u
M71 N026 A3 0 0 NMOS l=1u w=2u
M72 N026 B3 0 0 NMOS l=1u w=2u
M73 N031 A3 0 0 NMOS l=1u w=2u
M74 C3 C3_BAR 0 0 NMOS l=1u w=1u
M75 SUM_BAR2 C3_BAR N024 0 NMOS l=1u w=2u
M76 N024 A3 0 0 NMOS l=1u w=2u
M77 N024 B3 0 0 NMOS l=1u w=2u
M78 N024 C2 0 0 NMOS l=1u w=2u

```

M79 SUM_BAR2 C2 N025 0 NMOS l=1u w=3u
M80 N025 B3 N038 0 NMOS l=1u w=3u
M81 N038 A3 0 0 NMOS l=1u w=3u
M82 SUM3 SUM_BAR2 0 0 NMOS l=1u w=1u
M83 VDD SUM_BAR2 SUM3 VDD PMOS l=1u w=3u
M84 VDD C3_BAR C3 VDD PMOS l=1u w=3u
C14 SUM3 0 50p
C15 C3 0 50p
M85 VDD A4 N002 VDD PMOS l=1u w=6u
M86 VDD B4 N002 VDD PMOS l=1u w=6u
M87 VDD A4 N010 VDD PMOS l=1u w=6u
M88 N002 C3 C4_BAR VDD PMOS l=1u w=6u
M89 N010 B4 C4_BAR VDD PMOS l=1u w=6u
M90 VDD A4 N003 VDD PMOS l=1u w=6u
M91 VDD B4 N003 VDD PMOS l=1u w=6u
M92 VDD C3 N003 VDD PMOS l=1u w=6u
M93 N003 C4_BAR SUM_BAR3 VDD PMOS l=1u w=6u
M94 VDD A4 N001 VDD PMOS l=1u w=9u
M95 N001 B4 N016 VDD PMOS l=1u w=9u
M96 N016 C3 SUM_BAR3 VDD PMOS l=1u w=9u
M97 C4_BAR C3 N023 0 NMOS l=1u w=2u
M98 C4_BAR B4 N029 0 NMOS l=1u w=2u
M99 N023 A4 0 0 NMOS l=1u w=2u
M100 N023 B4 0 0 NMOS l=1u w=2u
M101 N029 A4 0 0 NMOS l=1u w=2u
M102 C4 C4_BAR 0 0 NMOS l=1u w=1u
M103 SUM_BAR3 C4_BAR N021 0 NMOS l=1u w=2u
M104 N021 A4 0 0 NMOS l=1u w=2u
M105 N021 B4 0 0 NMOS l=1u w=2u
M106 N021 C3 0 0 NMOS l=1u w=2u



```

```


M106 N021 C3 0 0 NMOS l=1u w=2u
M107 SUM_BAR3 C3 N022 0 NMOS l=1u w=3u
M108 N022 B4 N036 0 NMOS l=1u w=3u
M109 N036 A4 0 0 NMOS l=1u w=3u
M110 SUM4 SUM_BAR3 0 0 NMOS l=1u w=1u
M111 VDD SUM_BAR3 SUM4 VDD PMOS l=1u w=3u
M112 VDD C4_BAR C4 VDD PMOS l=1u w=3u
C19 SUM4 0 50p
C20 C4 0 50p
V5 A2 0 PULSE(0 3.3 0 10p 10p 20m 40m)
V6 B2 0 PULSE(0 3.3 0 10p 10p 10m 20m)
C6 A2 0 2p
C7 B2 0 2p
V7 A3 0 PULSE(0 3.3 0 10p 10p 80m 160m)
V8 B3 0 PULSE(3.3 0 0 10p 10p 40m 80m)
C8 A3 0 2p
C11 B3 0 2p
V9 A4 0 PULSE(0 3.3 0 10p 10p 40m 80m)
V10 B4 0 PULSE(3.3 0 0 10p 10p 40m 80m)
C12 A4 0 2p
C13 B4 0 2p
.model NMOS NMOS
.model PMOS PMOS
.lib C:\Users\Manoj Kumar Singh\Documents\
.tran 160m

```

(b)simulation results

 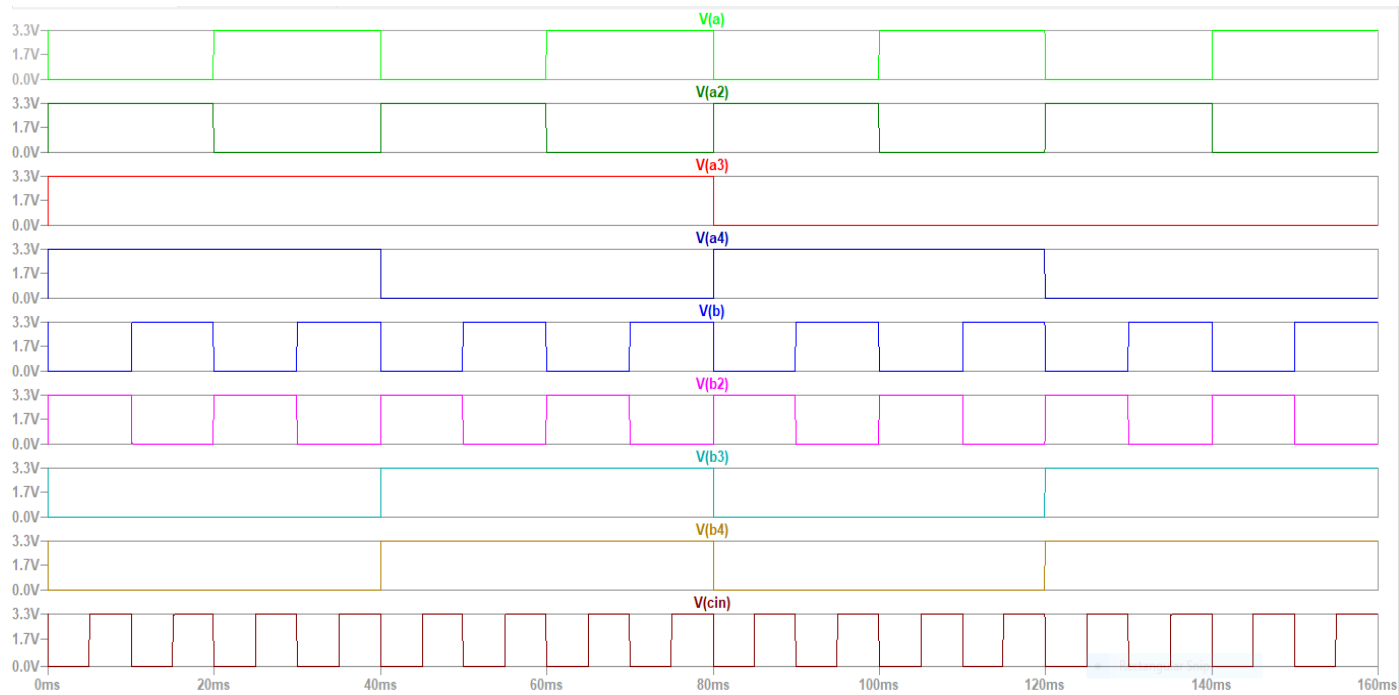

DELAY

 

As you can clearly see carry C3 comes before sum4. Similarly Cin, C1, C2, C3 comes before sum1, sum2, sum3 and sum4 respectively. So, our 4 bit ripple carry adder works perfectly.

DELAY IN CARRY C3=1063ns


DELAY IN SUM4=1310ns

Example: From 4bit RCA waveform , at the starting first edge:

	X4	X3	X2	X1
Cin				0
A	1	1	1	0
B	0	0	1	0
SUM	0	0	0	0
CARRY OUT	1	1	1	0

QUESTION 2: Design a superbuffer using CMOS inverters to drive a load of 100 fF, assume the input capacitance to be 2 fF.

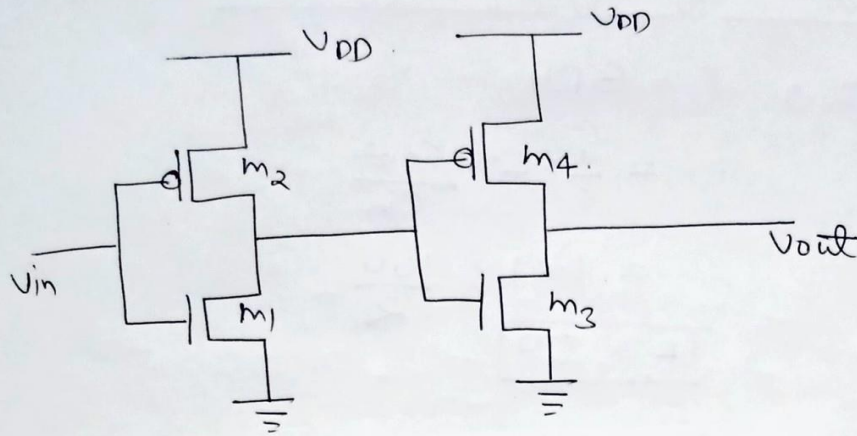(A) Detailed calculation and sizing of transistors



SUPER BUFFER

Regular CMOS inverter has pull up & pull down X-sistors. which do not have equal charging, discharging times when dealing with o/p capacitor due to inherent carrier mobility. Thus, having an inverter to drive any off-chip large cap or some other critical circuitry is not a reliable solution (asymmetric rise, fall delays).

In contrast to this super-buffers have good drive strength & provides symmetric driving behaviour (equal rise & fall times.) A super buffer has 4 internal X-sistors whose (W/L) ratios & connections gives better char. of charging/discharging o/p node cap. with symmetrical rise, fall delays.

By the method of Logical Effort:-

Path Effort, $F = GBH$.

$$= 1 \times 1 \times \frac{C_{out}}{C_{in}}$$

$$= 1 \times 1 \times \frac{160}{2}$$

$$\boxed{F = 50}$$

Best no. of stages, $\hat{N} = \log_4(F)$
 $= \log_4(50)$

$$\boxed{\hat{N} = 2.82}$$

For $N = 2$,

Delay, $d = NF^{1/N} + P$.

$$= 2(50)^{1/2} + 2$$

$$\boxed{d = 16.14 \text{ units}}$$

For $N = 3$,


$$d = NF^{1/N} + P$$

$$= 3(50)^{1/3} + 3$$

$$\boxed{d = 14.052}$$

So, for optimum/least delay we select $\boxed{N = 3}$ for our design.

 Calculation of parasitic capacitances & $(\frac{W}{L})$ ratio



$$\therefore \hat{f} = F_{NM} = g_1 h_1 = g_2 h_2 = g_3 h_3 \quad \text{--- (i)}$$

$$(i) \quad \therefore \hat{f} = g_3 h_3 \Rightarrow (50)^{1/2} = \sqrt{2 \times \frac{100}{C_n}}$$

$$C_n = \frac{100}{3.68}$$

$$\boxed{C_n = 27.14 \text{ fF}}$$

Now,

$$\text{For Level 3, } \mu_n : \mu_p = 660 : 210$$

$$= 3.14 : 1$$

$$\boxed{\mu_n : \mu_p \approx 3 : 1}$$

$$\therefore (L \cdot C_{ox})(4W) = C_n$$

$$\Rightarrow (1 \times 10^{-6}) (24.65 \times 10^{-4})$$

$$= 27.14 \times 10^{-15}$$

$$\Rightarrow W = 2.755 \times 10^{-6}$$

$$\boxed{W = 2.755 \mu\text{m}}$$

$$C_{ox} = \frac{\epsilon_0 \epsilon_{ox}}{t_{ox}}$$

$$= \frac{3.9 \times 8.85 \times 10^{-12}}{1.4 \times 10^{-8} \text{ m}}$$

$$\boxed{C_{ox} = 24.65 \times 10^{-4} \text{ f/m}^2}$$

$$\text{P-mos}_3 \Rightarrow 3W = 8.25 \mu\text{m}$$

$$\text{Nmos}_3 \Rightarrow 1W = 2.75 \mu\text{m}$$

--- (ii)

$$(ii) \quad f = g_m h_2 \Rightarrow 3.68 = 1 \times \frac{C_m}{C_y}$$

$$C_y = \frac{27.14}{3.68}$$

$$C_y = 7.375 \text{ fF}$$

Now,

$$(L \cdot C_{ox}) 4n = 7.375 \text{ fF}$$

$$(1 \times 10^{-6}) \times (24.65 \times 10^{-4}) \cdot (4n) = 7.375 \times 10^{-15}$$

$$n = \frac{7.375 \times 10^{-15}}{1 \times 10^{-6} \times 24.65 \times 10^{-4}} = 0.748 \mu\text{m}$$

$\text{Pmos} \Rightarrow 3n = 2.22 \mu\text{m}$ $\text{Nmos} \Rightarrow n = 0.748 \mu\text{m}$
--

$$(iii) \quad f = g_m h_1 \Rightarrow 3.68 = 1 \times \frac{C_y}{C_a}$$

$$C_a = \frac{7.375}{3.68} = 2 \text{ fF}$$

$$\therefore (L \cdot C_{ox}) 4n = 2 \text{ fF}$$


$$(1 \times 10^{-6}) \times (24.65 \times 10^{-4}) (4n) = 2 \times 10^{-15}$$

$$n = 0.202 \mu\text{m}$$

$\therefore \text{Pmos} \Rightarrow 3n = 0.608 \mu\text{m}$ $\text{Nmos} \Rightarrow n = 0.202 \mu\text{m}$
--

(B)SPICE NETLIST

❖ Without optimisation

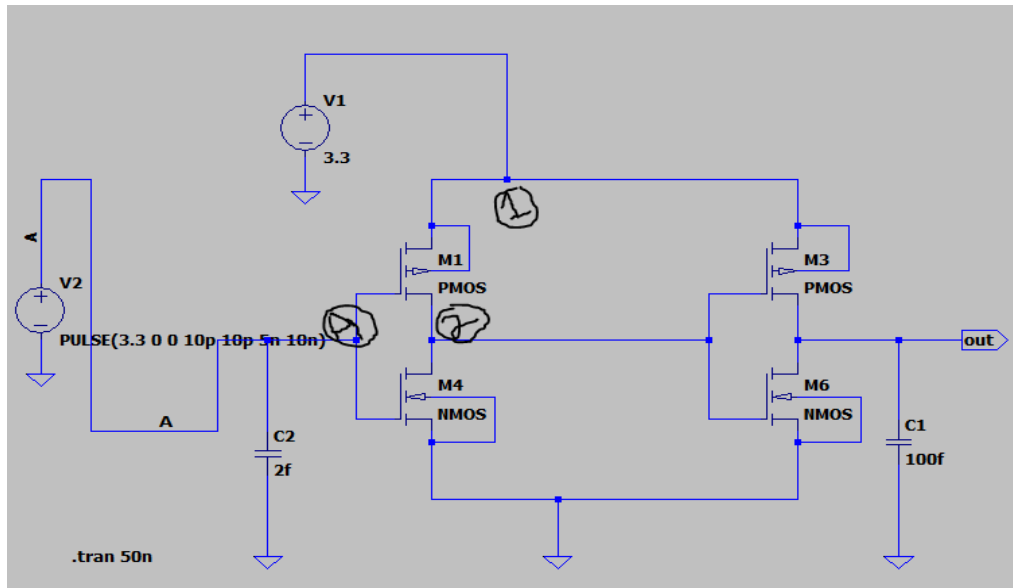


```
M1 1 A 2 1 PMOS l=1u w=3u
M3 1 2 out 1 PMOS l=1u w=3u
M6 out 2 0 0 NMOS l=1u w=1u
M4 2 A 0 0 NMOS l=1u w=1u
V1 N001 0 3.3

V2 A 0 PULSE(3.3 0 0 10p 10p 5n 10n)
C1 out 0 100f
C2 A 0 2f

.model NMOS NMOS
.model PMOS PMOS
.tran 50n
```

❖ Optimised

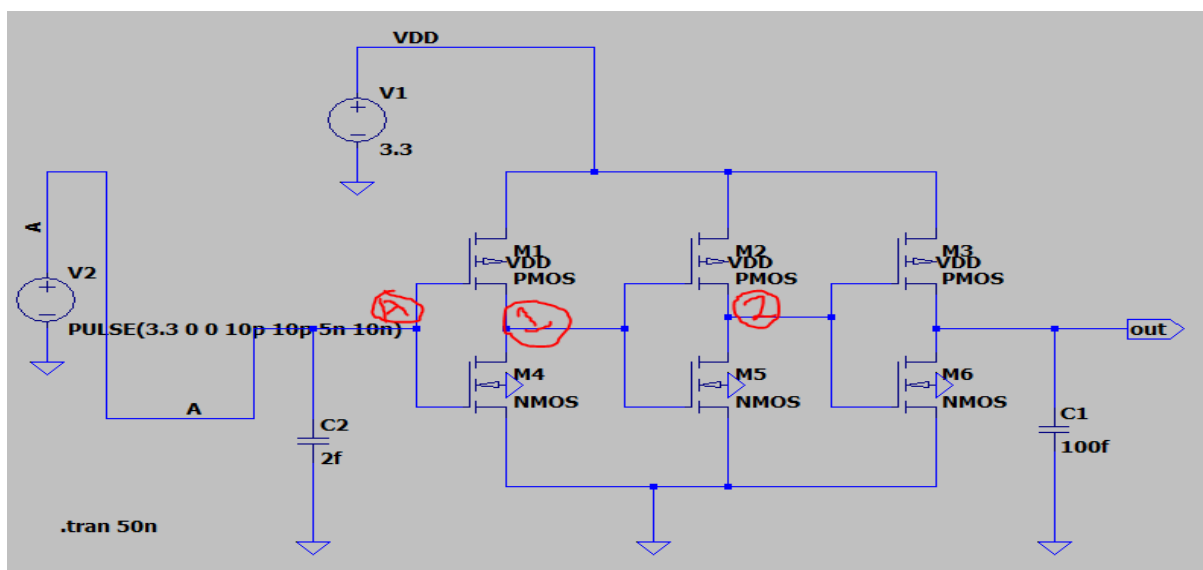


```

M1 VDD A 1 VDD PMOS l=1u w=0.61u
M2 VDD 1 2 VDD PMOS l=1u w=2.22u
M3 VDD 2 out VDD PMOS l=1u w=8.25u
M5 2 1 0 0 NMOS l=1u w=0.75u
M6 out 2 0 0 NMOS l=1u w=2.75u
M4 1 A 0 0 NMOS l=1u w=0.20u



V1 VDD 0 3.3
V2 A 0 PULSE(3.3 0 0 10p 10p 5n 10n)

C1 out 0 100f
C2 A 0 2f


.model NMOS NMOS
.model PMOS PMOS
.tran 50n

```

  (C) Simulation result and calculation of delay



FALL DELAY=1.581ns

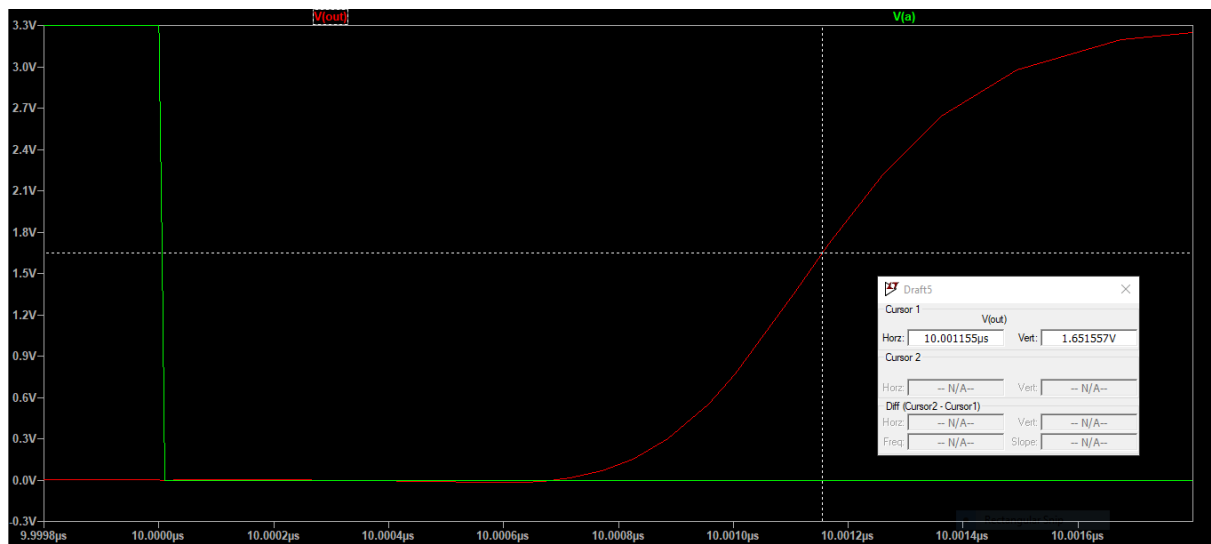

RISE DELAY=1.155ns